 


FPGA-Based Hardware Implementation of a Scalable, Streaming Split-Radix FFT Processor


Christodoulos Zerdalis
03531

Classic Split-Radix




- **L-shaped** geometry
- Very **irregular pattern** for an **SDF** implementation
- **Butterfly** supports only **two samples** per clock

Revised Split-Radix

 

- **Symmetrical geometry down the middle**
- More **regular structure** that supports **four samples per clock**.

Revised Butterfly

 

- **Four samples** per iteration
- Does **not** use **multiplication**, these **happen independently**


Hardware Design

Overview


We will implement **five different** hardware **stages** to accommodate the **complexity** of the **split-radix** algorithm.

The **third stage** is the **scalable** one, while the **others** are designed to handle **exceptions** in the pattern.

N times

 


Decomposition into stages

 


STAGE 1

- Does not have any multiplications
- This structure closely resembles the Radix-4 architecture


Top diagram 1st stage

 

Memory pattern 1st stage

 


Input pattern

 


Output pattern


Memory pattern 1st stage

 

Memory pattern general diagram

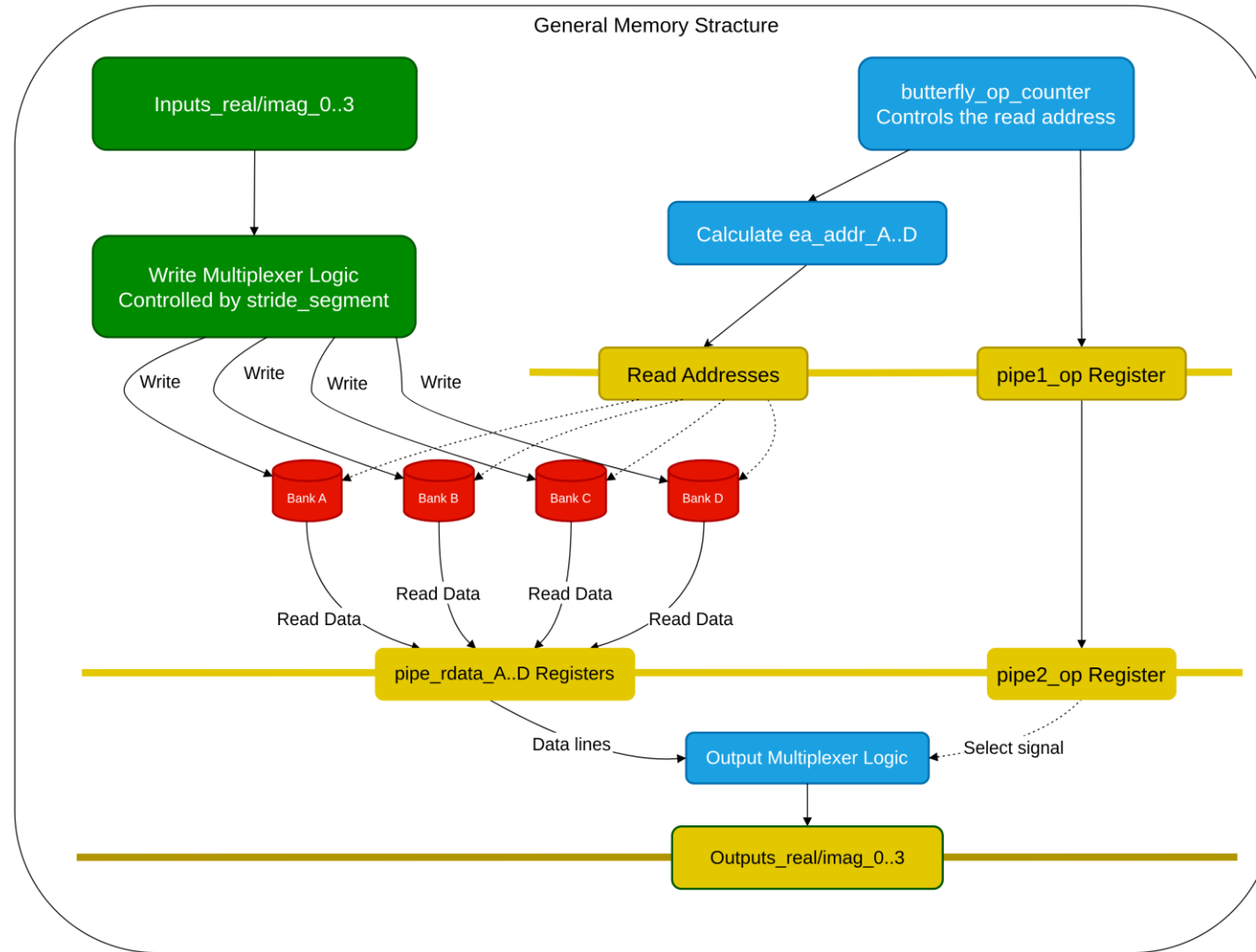


Decomposition into stages

 

STAGE 2


- First multiplications
- New structure/architecture

Memory pattern 2nd stage

 

Input pattern

 
Upper and lower inputs
get multiplied before
memory



Input pattern Start of output

Middle inputs go to
memory for the first
half, and then pass
through to the butterfly


Memory pattern 2nd stage

 

End of output

Memory outputs the
stored results of the
multiplications

Top diagram 2nd stage

 


Memory pattern 2nd stage


BANK A	BANK B	BANK C	BANK D
MU1	B2	ML3	B4
B8	MU5	B6	ML7
ML11	B12	MU9	B10
B14	ML15	B16	MU13
MU17	B18	ML19	B20
B24	MU21	B22	ML23
ML27	B28	MU25	B26
B30	ML31	B32	MU29

Memory pattern 2nd stage

BANK A	BANK B	BANK C	BANK D
MU1	MU33	ML3	ML35
ML39	MU5	MU37	ML7
ML11	ML43	MU9	MU41
MU45	ML15	ML47	MU13
MU17	MU49	ML19	ML51
ML55	MU21	MU53	ML23
ML27	ML59	MU25	MU57
MU61	ML31	ML63	MU29

 


Decomposition into stages

 

STAGE 3

- Stage 3 is the stage that can make the design scalable and sits after the first two but before the last two stages
- Needs more complex controls, is not visible here as it is needed for ffts larger than 64 samples


Stage 3 "steps" explained

 

STAGE 3

- The red square indicates step 0
- The green ones step 1
- The current's stages step mode is decided by the counters in the control unit plus the stepmode of the previous stage


Top diagram 3rd stage

 


Memory pattern 3rd stage

The **memory** in this stage is a **combination** of the **first** and **second** stage's **memories** since step 0 and step 1 **closely match** stage 1 and 2


FSM 3rd stage

 

Processing state diagram

 


Decomposition into stages

 

STAGE 4 (second to last)

- The same exact logic as stage 3 uses the same FSM but the memory is not compatible
- For this stage i implement the delays with shift registers instead of memory that is compatible with bram , since the delays are fixed and small


Top diagram 4th stage

 

In this design, we can see that the **multipliers** and **butterfly** units work in **parallel**, rather than **sequentially** as in the **previous** stages.

Each delay cycle is **exactly** what the data needs to be correctly **aligned** at the **butterfly** input and the stage **output**.


Decomposition into stages

 

STAGE 5 (last)

- The same exact logic as stage 3 and 4 uses a simpler FSM
- In this stage i combine the last two stages of the algorithm since the last stage is very simple (only one +/-)

Top diagram 5th stage

 

In this design, we can see that the **multipliers** and **butterfly** units work in **parallel** again.

At the end there is an extra **adder** for the **last stage** of the algorithm

Two types of complex multiplication modes

Simple multiplication

Uses 8 multipliers

```
always@(posedge clock) begin
    rr_a <= a_re * w0re;
    ii_a <= a_im * w0im;
    ri_a <= a_re * w0im;
    ir_a <= a_im * w0re;

    rr_b <= b_re * wlre;
    ii_b <= b_im * wlim;
    ri_b <= b_re * wlim;
    ir_b <= b_im * wlre;

    out_a_re <= rr_a - ii_a;
    out_a_im <= ri_a + ir_a;
    out_b_re <= rr_b - ii_b;
    out_b_im <= ri_b + ir_b;
end
```

Cheap multiplication

Uses 6 multipliers

```
always @(posedge clock) begin
    sum_a_in <= a_re + a_im;
    sum_w0_in <= w0re + w0im;
    diff_w0_in <= w0im - w0re;
    sum_b_in <= b_re + b_im;
    sum_w1_in <= wlre + wlim;
    diff_w1_in <= wlim - wlre;
    a_re_d <= a_re;
    a_im_d <= a_im;
    w0re_d <= w0re;
    b_re_d <= b_re;
    b_im_d <= b_im;
    wlre_d <= wlre;

    k1_a <= w0re_d * sum_a_in;
    k2_a <= a_re_d * diff_w0_in;
    k3_a <= a_im_d * sum_w0_in;

    k1_b <= wlre_d * sum_b_in;
    k2_b <= b_re_d * diff_w1_in;
    k3_b <= b_im_d * sum_w1_in;

    out_a_re <= k1_a - k3_a;
    out_a_im <= k1_a + k2_a;

    out_b_re <= k1_b - k3_b;
    out_b_im <= k1_b + k2_b;
end
```

Based on **Gauss's** complex multiplication

Results

Table 1: Synthesis Results for 256-point Split-Radix FFT

Design	LUTs	Registers	Clock (ns)	BRAMs	DSPs
Cheap Mult	6586	7518	10.00	0	36
Simple Mult	6581	7004	10.00	0	48

The 'Cheap Mult' version utilizes fewer DSPs however, it requires more registers due to the additional pipeline that the cheap mult module needs.